

How My DIY RFID Reader Became a Lifesaver

SecretCon 2 | Dale Cook





■ whoami

- D0zer aka Decrazyo
- Penetration tester
 - OSCP, OSCE, OSWE certified
- Exploit developer
 - I'll use any language but Java
- Electronics hobbyist
 - Not an electrical engineer!

Background





Cinnamon Bun




Huntress Wizard



Background

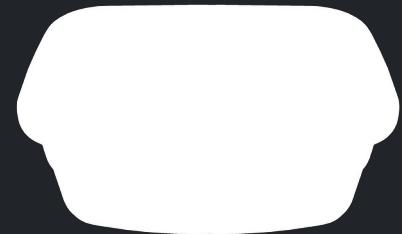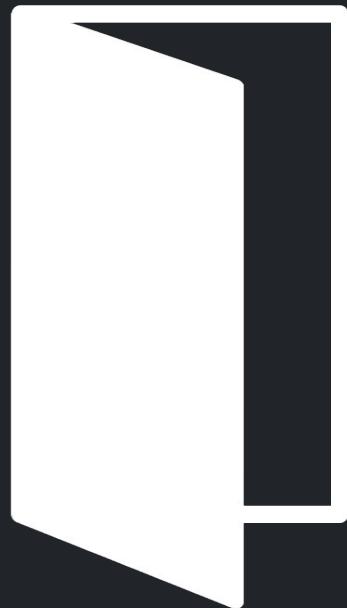

Background

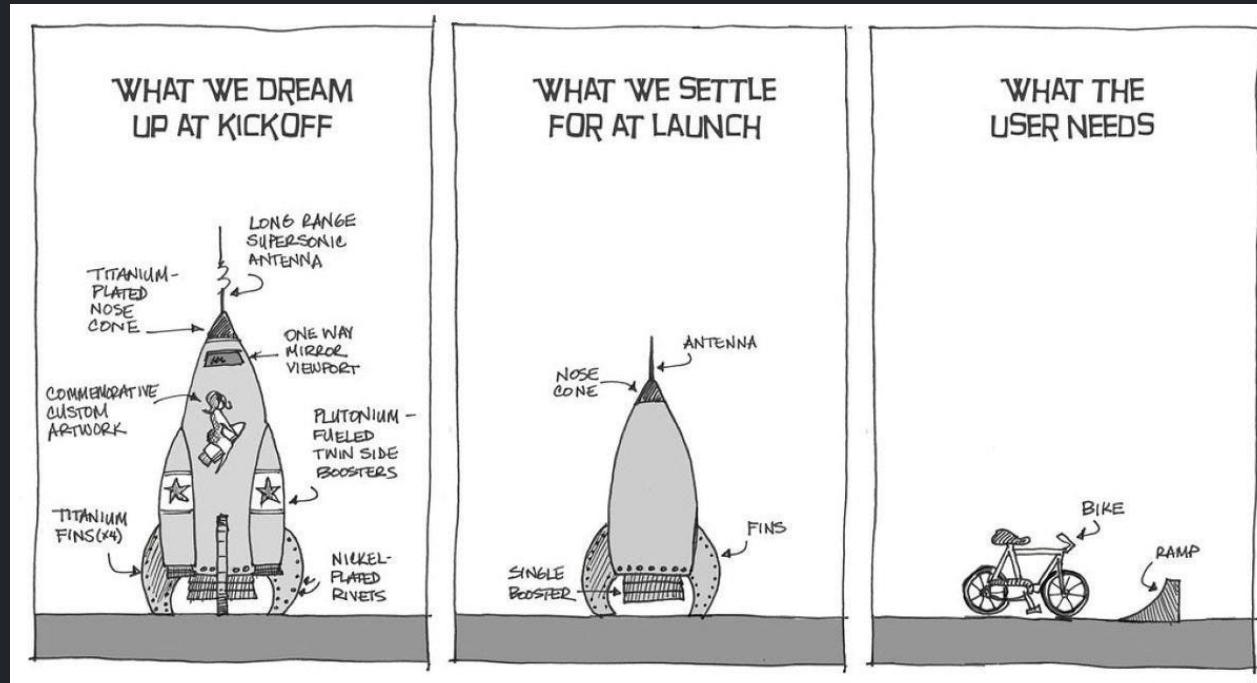

Background

Spoiler alert

It didn't work

Background

1) RFID is short range



2) Cats are jerks



RFID Tag

- Glass capsule

- Antenna coil

- Integrated circuit

- Non-volatile memory

- Transmitter logic




RFID Reader

- Power
- Clock signal
- Communication channel



RFID Reader

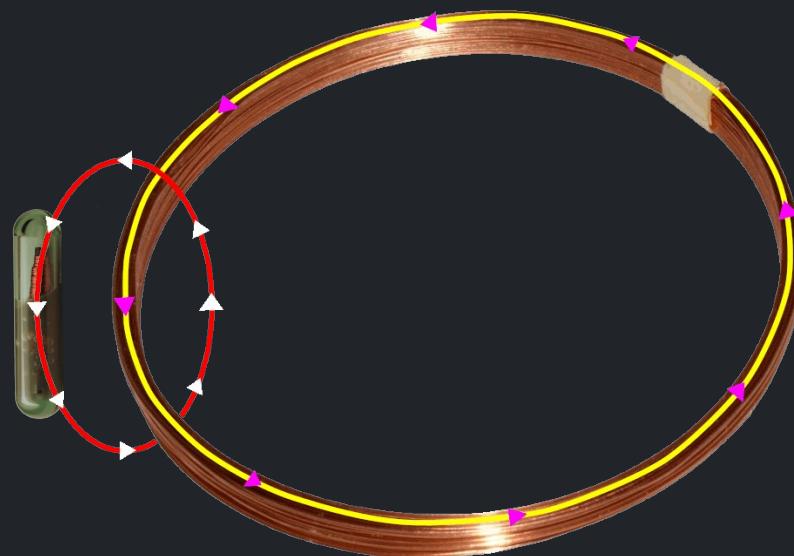- Power
- Clock signal
- Communication channel



RFID Reader

- Power
- Clock signal
- Communication channel



RFID Reader



- 5V Arduino Nano @ 16MHz


RFID Reader



134.2kHz
134.4kHz


- 5V Arduino Nano @ 16MHz
- Pulse width modulation (PWM)
- 16-bit timer

RFID Reader

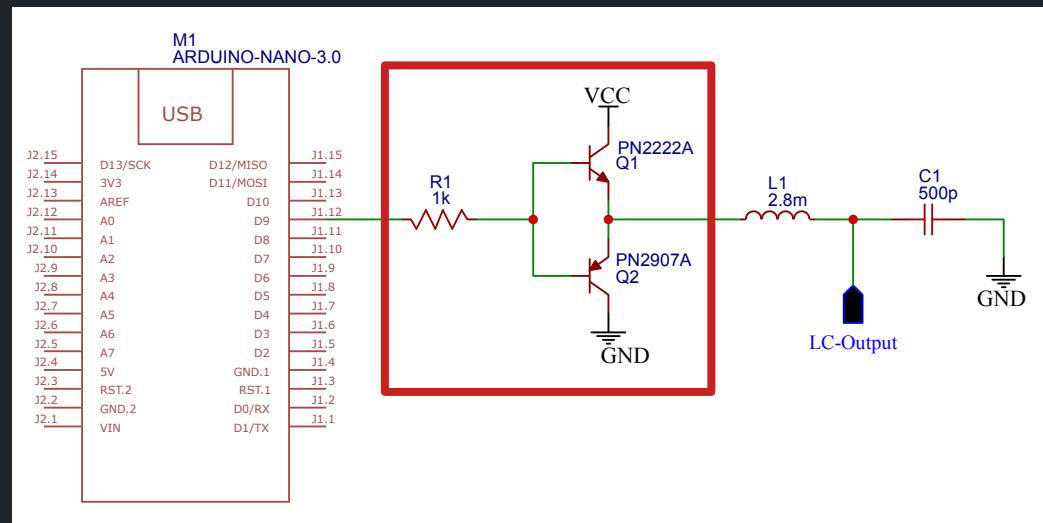


■ Push-pull amplifier

RFID Reader

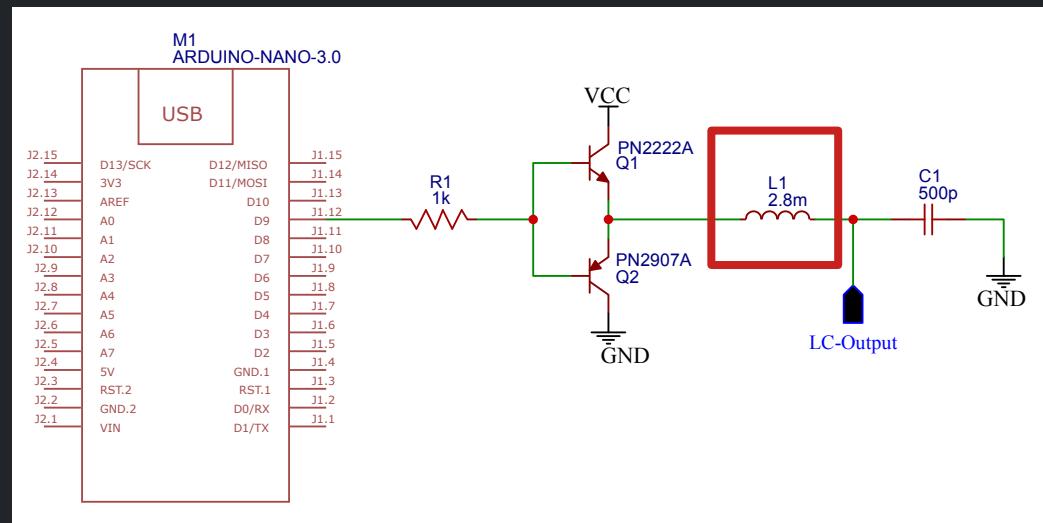

- Push-pull amplifier
- Antenna coil

RFID Reader

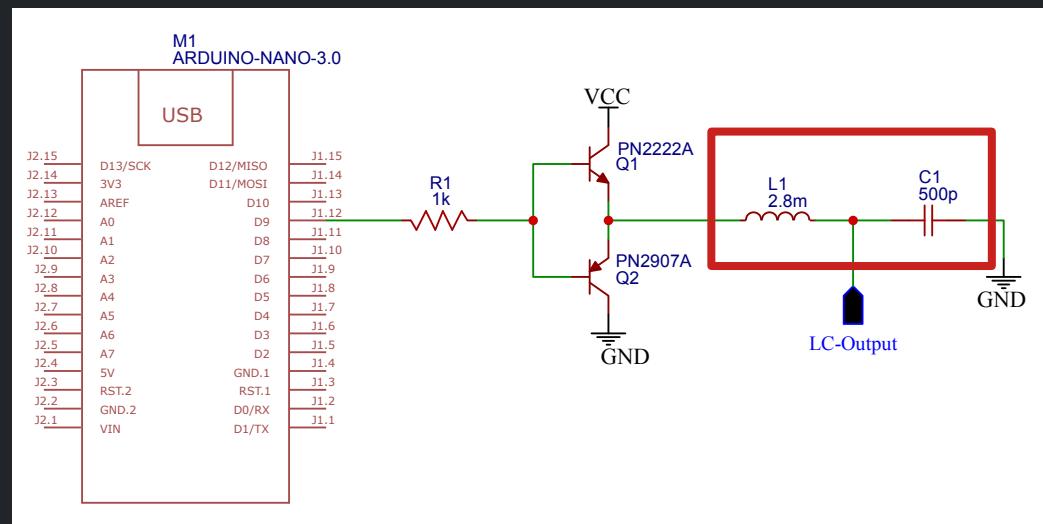

- Push-pull amplifier

- Antenna coil


- LC resonator

- $$f = \frac{1}{2\pi\sqrt{L \times C}}$$


- $$134.40 \text{ kHz} \approx \frac{1}{2\pi\sqrt{2.8 \text{ mH} \times 500 \text{ pF}}}$$

RFID Reader

Reader antenna

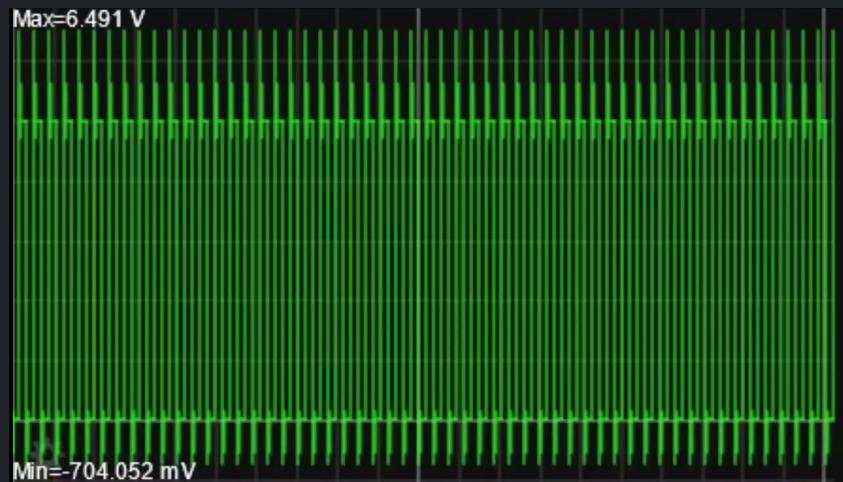


Reader antenna with tag

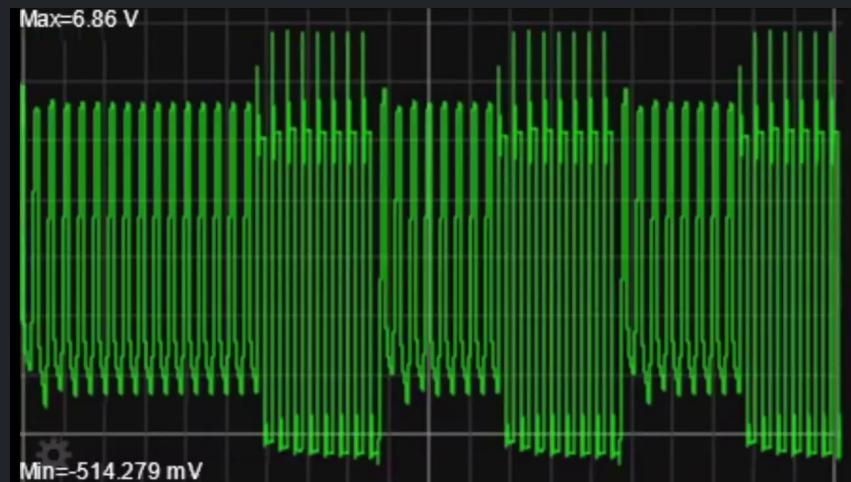



Modulation

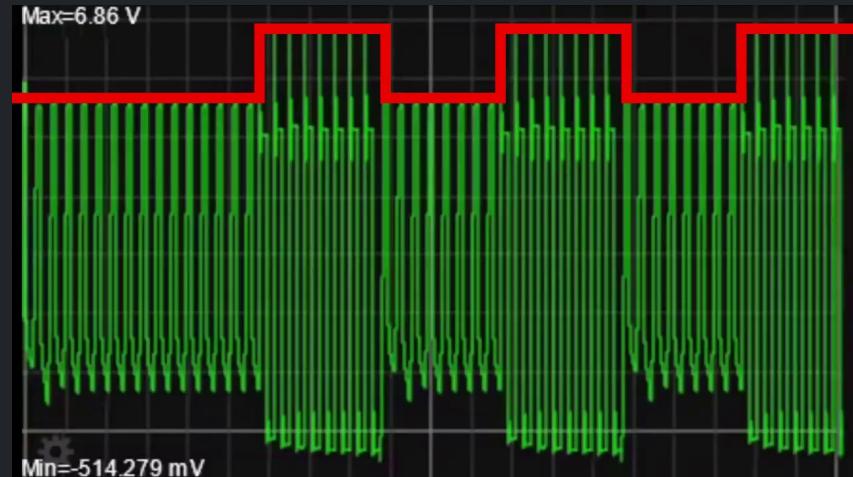- Amplitude shift keying (ASK)
 - AM radio
 - Digital data




Encoding

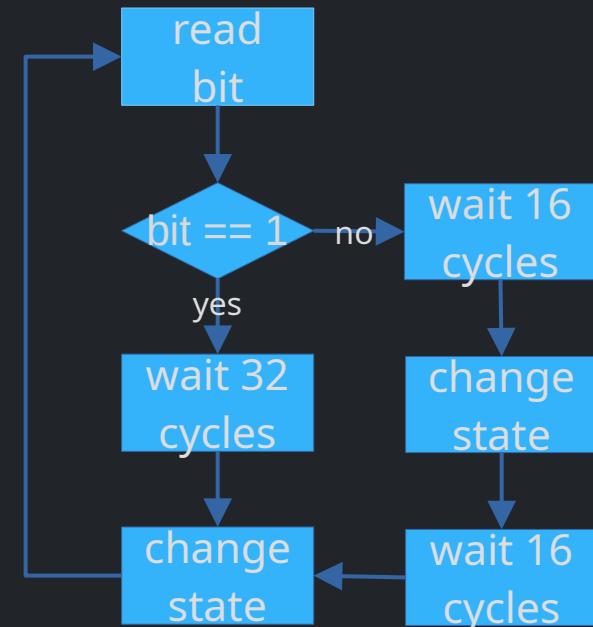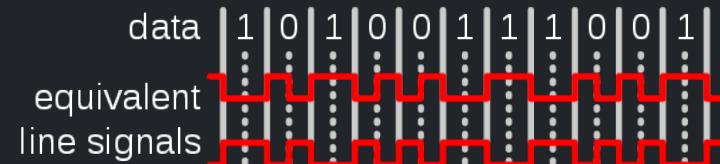- Differential Manchester
- 32 cycle bit period
 - Data signal frequency $8.4 \text{ kHz} = \frac{134.4 \text{ kHz}}{16}$




Demodulation

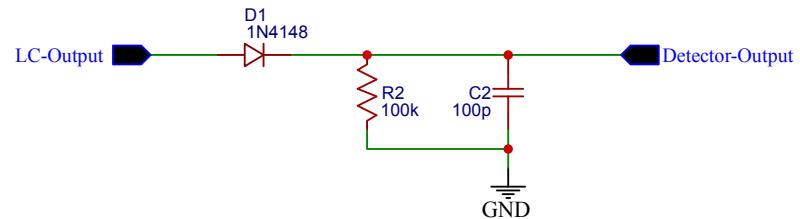


■ Envelope detector

Demodulation

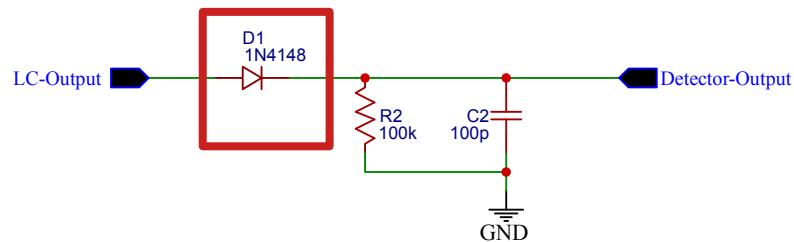

- Envelope detector
- Fast switching diode


Demodulation

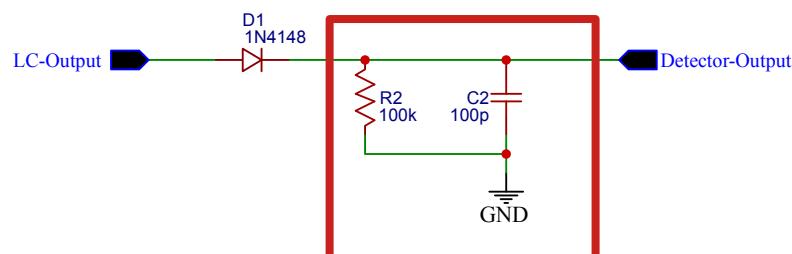


- Envelope detector
- Fast switching diode
- RC filter
 - $\frac{1}{134.4 \text{ kHz}} < \tau < \frac{1}{8.4 \text{ kHz}}$
 - $\tau = 0.1 \times \frac{1}{8.4 \text{ kHz}} = 11.9 \mu\text{s}$
 - $\tau = R \times C$
 - $11.9 \mu\text{s} \approx 100 \text{ k}\Omega \times 100 \text{ pF}$

Demodulation


Reader antenna with tag (input)

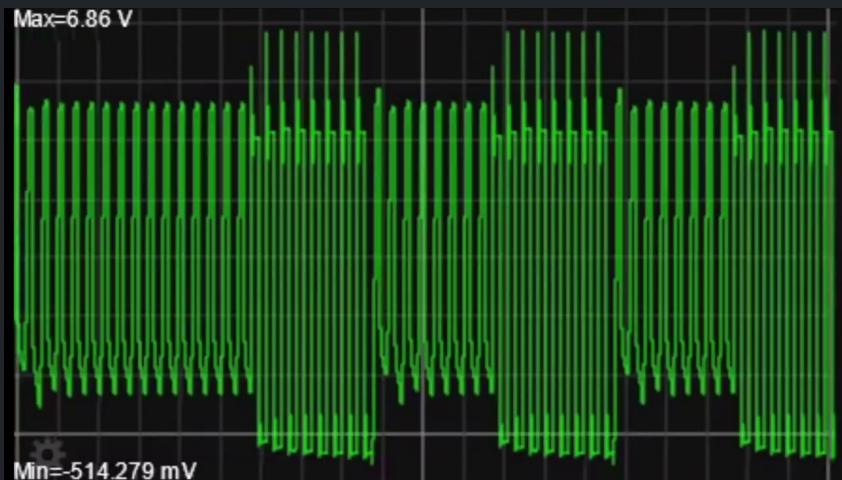

Envelope detector (output)

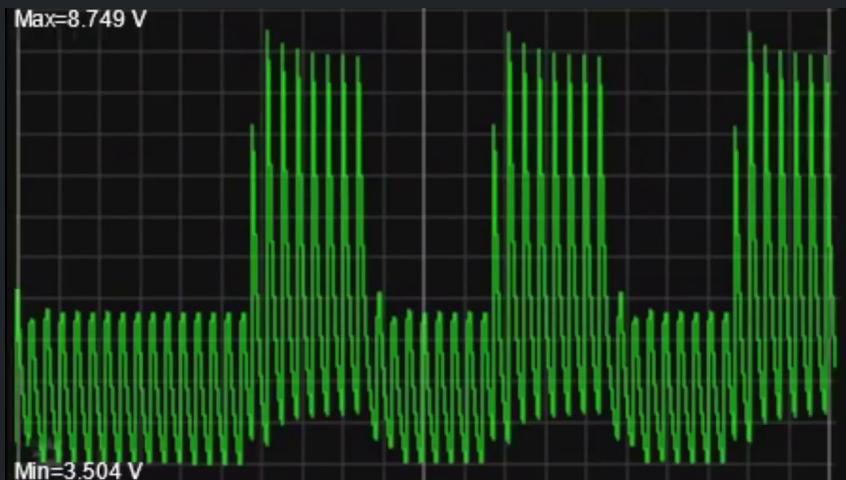

Filtering

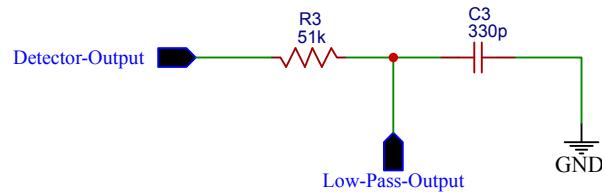

- Low-pass filter

- $$f = \frac{1}{2\pi \times R \times C}$$

- $$8.4 \text{ kHz} \approx \frac{1}{2\pi \times 51 \text{ k}\Omega \times 330 \text{ pF}}$$

Filtering


Envelope detector (input)



Low-pass filter (output)




Amplification

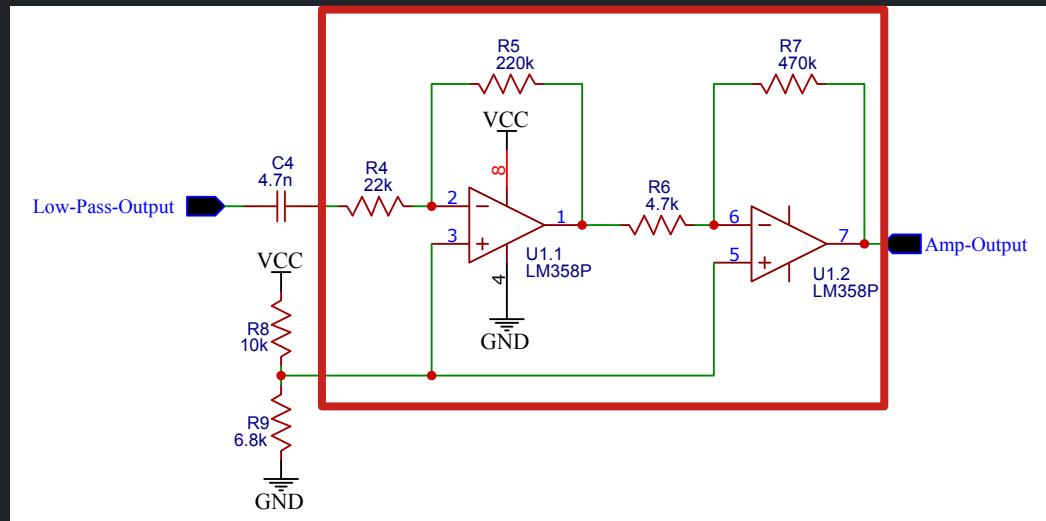


- Operational Amplifiers (op-amps)
 - Inverting configuration

Amplification

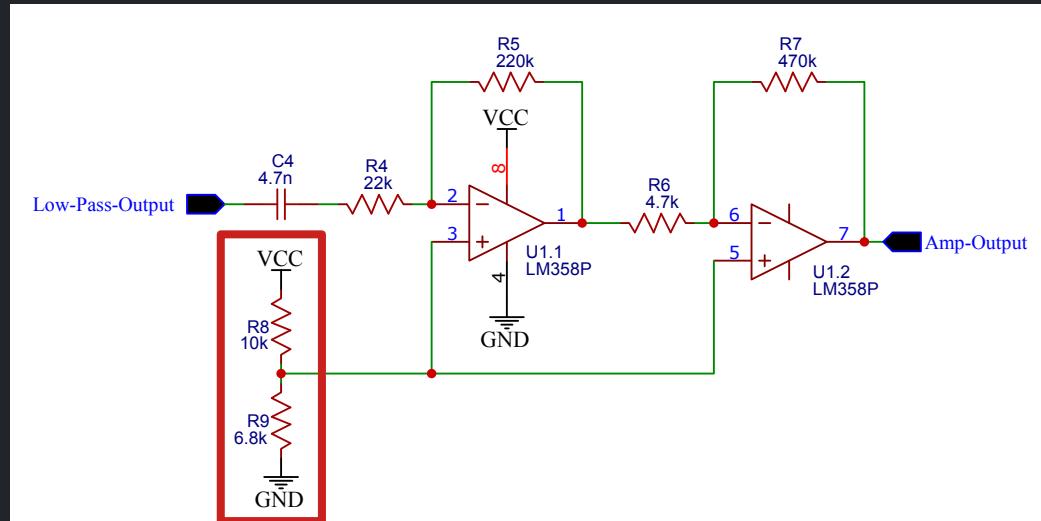

- Operational Amplifiers (op-amps)
 - Inverting configuration
- Voltage divider
 - Op-amp set point

Amplification

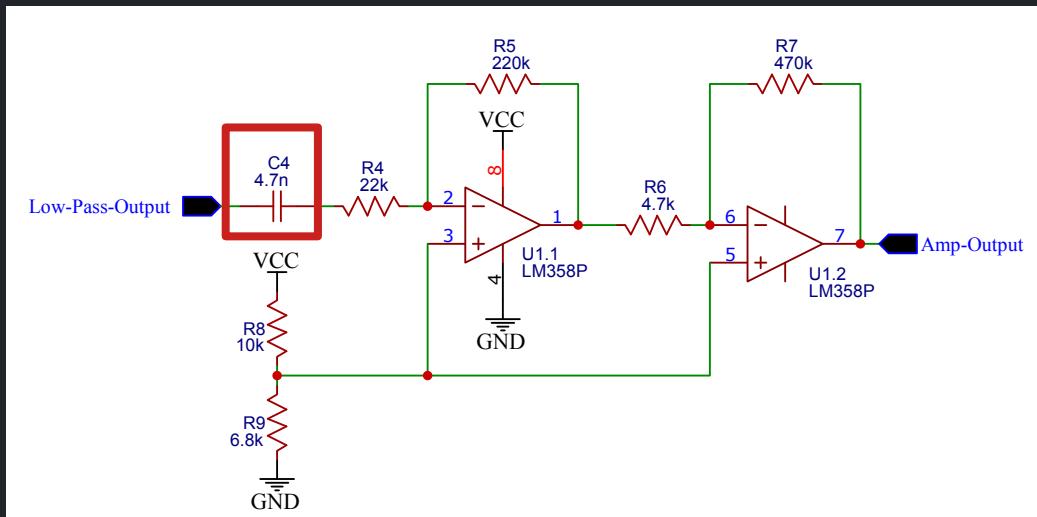


- Operational Amplifiers (op-amps)
 - Inverting configuration
- Voltage divider
 - Op-amp set point
- Series capacitor
 - Oscillate around set point

Amplification

Low-pass filter (input)



Op-amps (output)

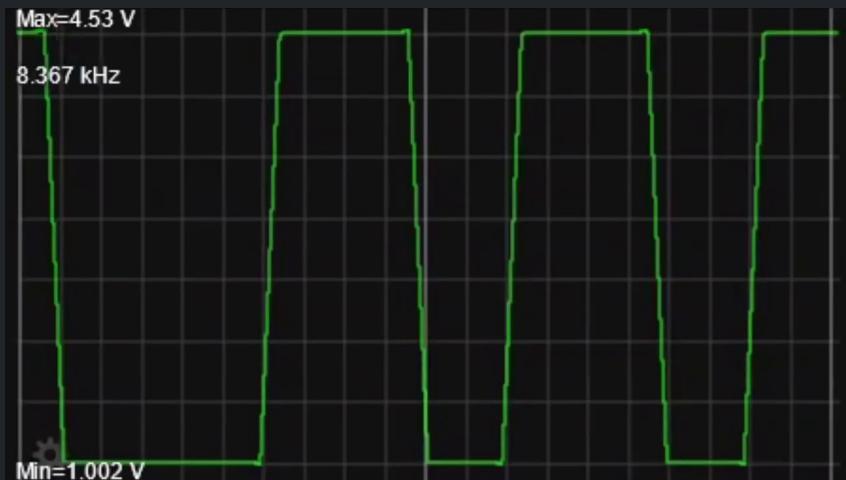

Decoding

- Record time between pin changes

10	140	49	120	119	239	240	118	119	238	120	118	119	119	238	239
----	-----	----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----


- Divide by half bit period

- $119.04 \mu s = \frac{1}{8.4 \text{ kHz}}$

$$y = \frac{x}{119.04 \mu s}$$

- 1, 1 → 0

- 2 → 1

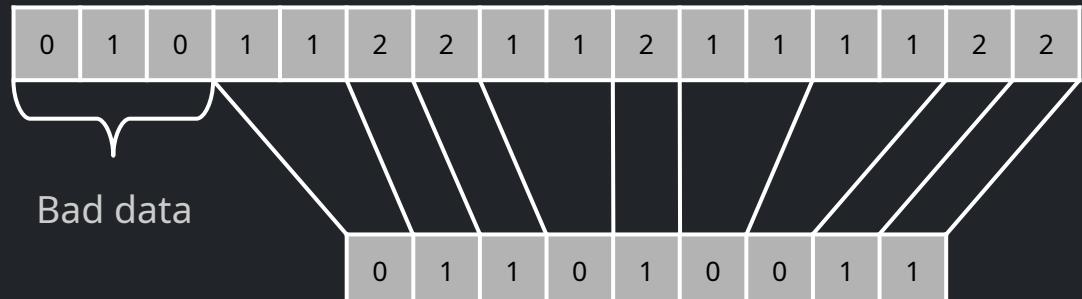

Parsing

- 11-bit header

LSB	MSB
00000000001	
000011111	
110000001	
000000001	
000000001	
000000111	
100111111	
1-----1	
-----11	
011010111	
101110101	
011010101	
001011001	
010010001	


Parsing

- 11-bit header
- Control bits

LSB	MSB
00000000001	
000011111	
1100000001	
0000000001	
0000000001	
0000000001	
0000000001	
100111111	
1-----1	
-----11	
011010111	
101110101	
011010101	
001011001	
010010001	


Parsing

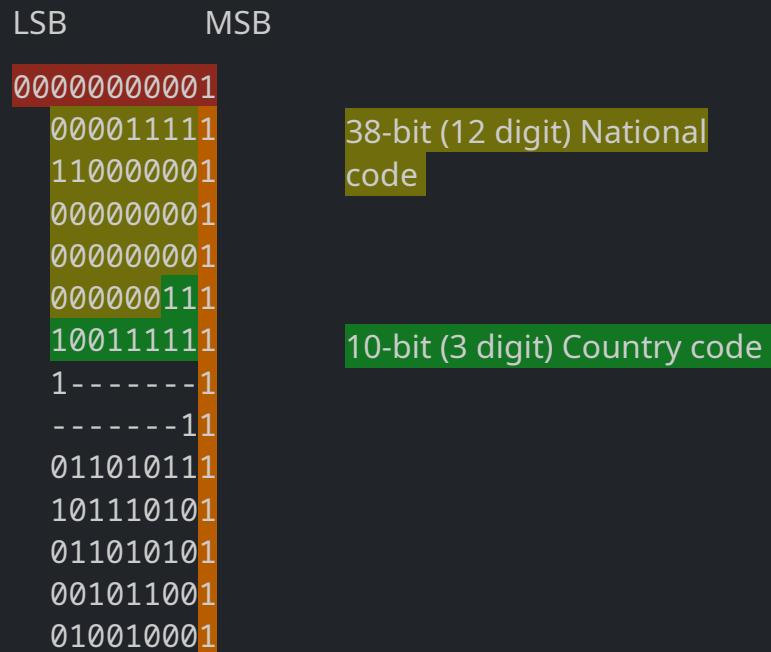- 11-bit header
- Control bits
- 48-bit (15 digit) unique ID




Parsing

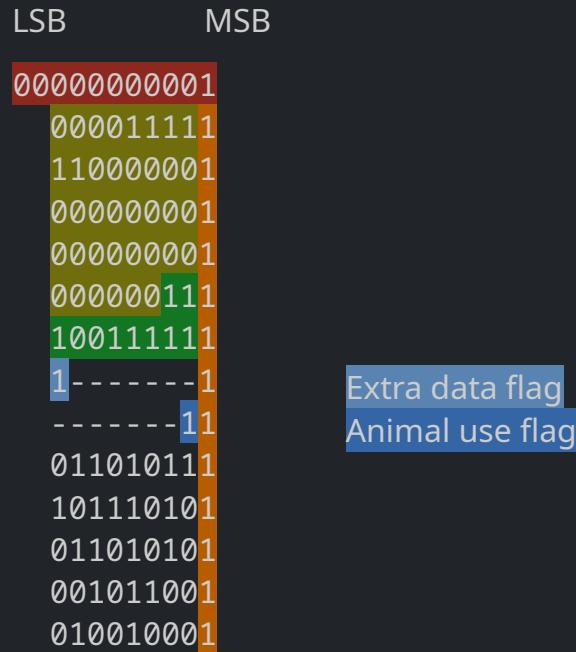- 11-bit header
- Control bits
- 48-bit (15 digit) unique ID
- Flags




Parsing

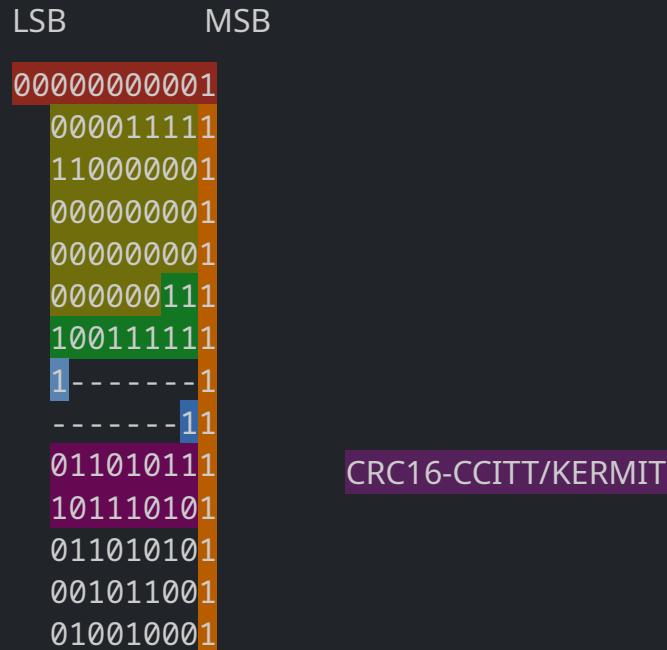- 11-bit header
- Control bits
- 48-bit (15 digit) unique ID
- Flags
- Checksum




Parsing

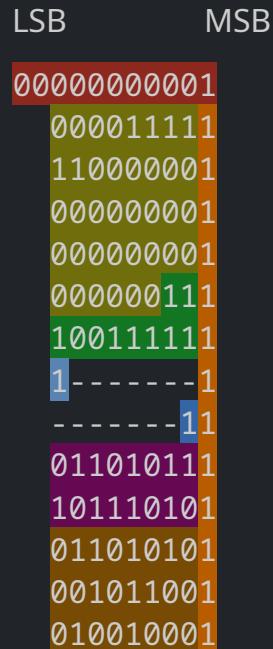- 11-bit header
- Control bits
- 48-bit (15 digit) unique ID
- Flags
- Checksum
- Extra data



Demo time

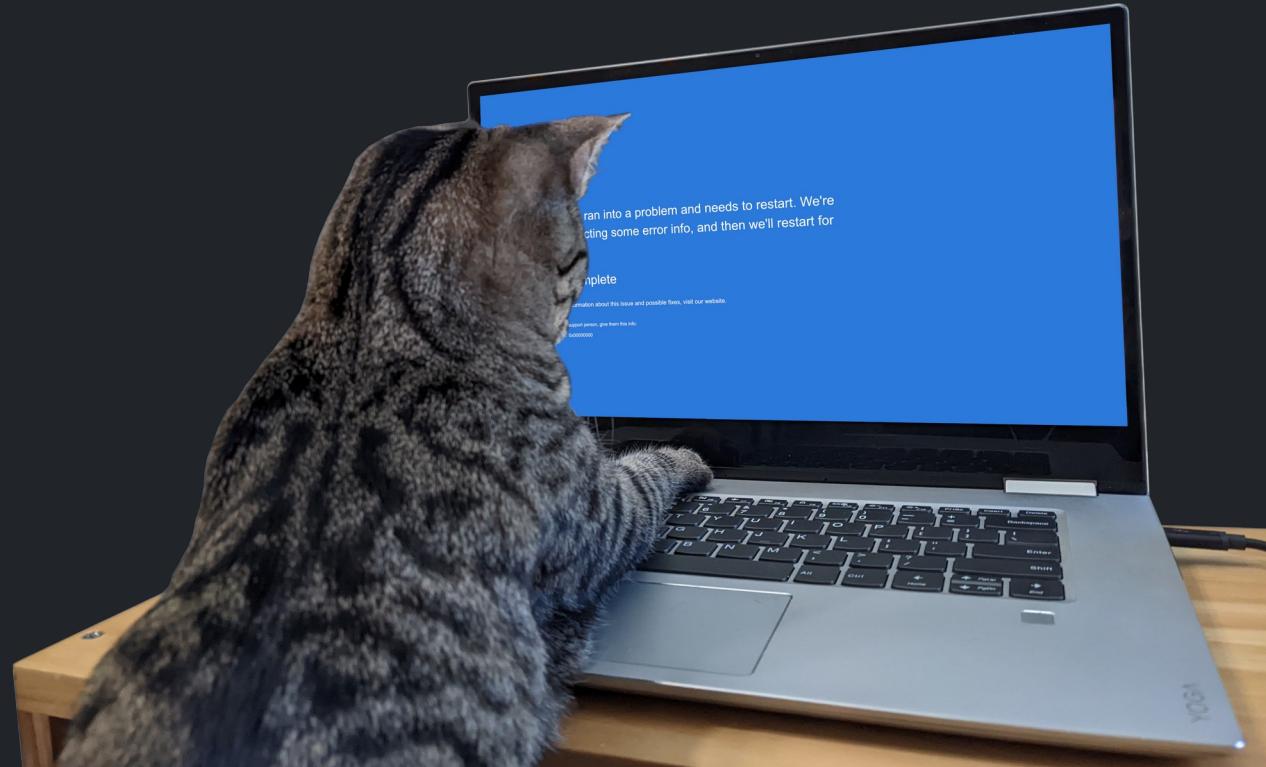

Story time

- Tested on bare RFID tags

- It works!

```
Ready!
Success!
981020037449754
This tag is intended for animal use
=====
```

- Tested on cats

- It works?

```
Success!
981020037449754
This tag is intended for animal use
=====
```

```
Success!
981020037449754
This tag is intended for animal use
=====
```

```
Success!
981020037449754
This tag is intended for animal use
```

Story time

Microchip	981020037449854
Name	Huntress Wizard
Species	Feline/Cat
Breed(s)	Shorthair

Ready!

Success!

981020037449754

This tag is intended for animal use

=====

Success!

981020037449754

This tag is intended for animal use

=====

Success!

981020037449754

This tag is intended for animal use

=====

Success!

981020037449754

This tag is intended for animal use

Story time

Microchip	981020037449854
Name	Huntress Wizard
Species	Feline/Cat
Breed(s)	Shorthair

Ready!

Success!

981020037449764

This tag is intended for animal use

Success!

981020037449754

This tag is intended for animal use

Success!

981020037449754

This tag is intended for animal use


Success!

981020037449754

This tag is intended for animal use

Pet Microchip Registrations

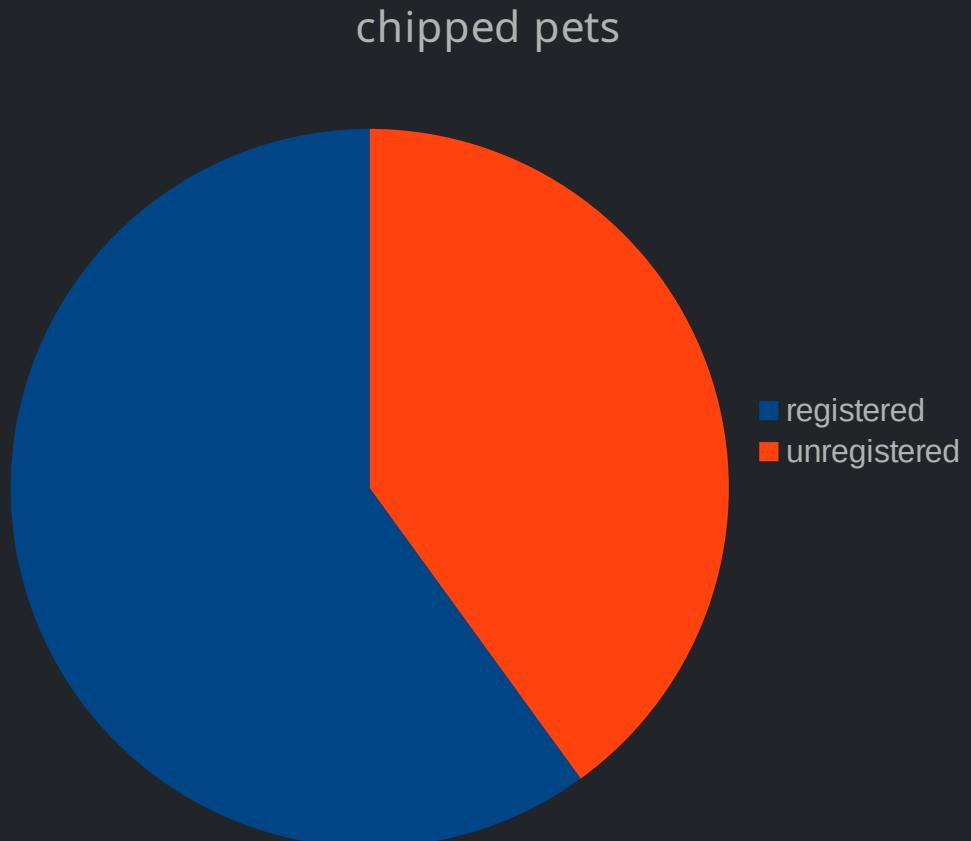40% of microchipped pets are
“unregistered”.



Pet Microchip Registrations

40% of microchipped pets are “unregistered”.

Some “unregistered” pets are the result of clerical errors.



Lessons for engineers

- Humans suck!!!
- Checksums rule!
- So do parity bits!




Lessons for pet owners

- Check the chip!



Lessons for pet owners

- Check the chip!
 - Flipper

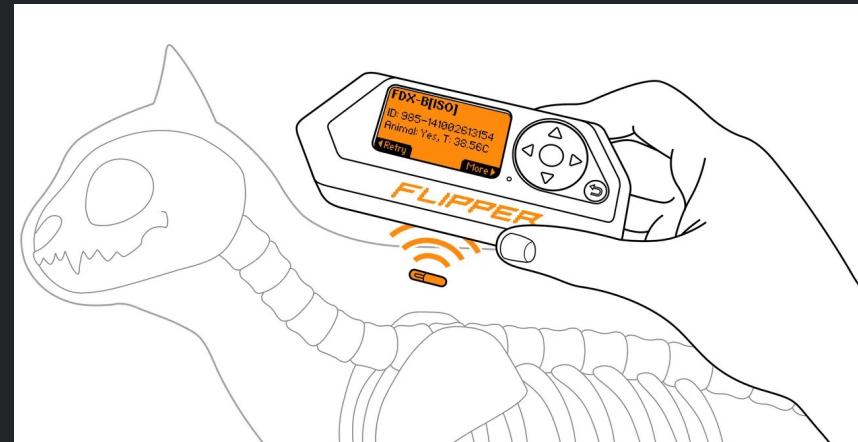

Lessons for pet owners

- Check the chip!
 - Flipper
 - Ask your vet





Thank You

SecretCon 2 | Dale Cook

<https://github.com/decrazyo/fdxb>

<https://www.youtube.com/@decrazyo>

